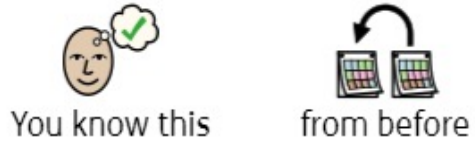


Prior Learning





Common appliances that run on electricity




Common conductors


Common insulators

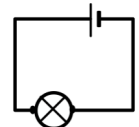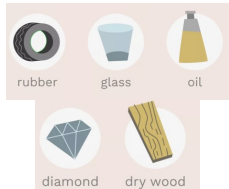

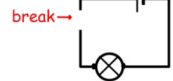Complete circuits have no breaks in them, allowing electricity to run freely.





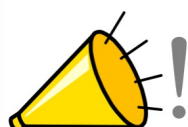Incomplete circuits have a break in them, stopping electricity running freely.



Turning up the volume. Higher voltage = louder sound.


Basic parts of a circuit

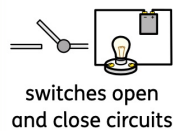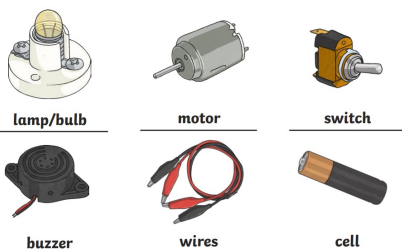


Vocabulary

material	attract	repel
static	rub	electricity
charged	components	complete circuit
current	brighter	duller
voltage	series circuit	parallel circuit
appliance/device	conductor	insulator
metals	non-metals	positive
negative	resistance	crocodile clips




Electricity

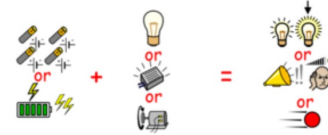

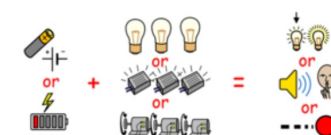More cells, or a higher voltage cell = bulbs brighter, motors faster and buzzers louder.



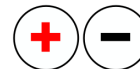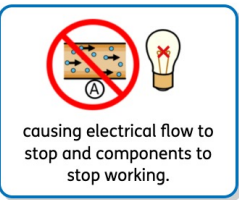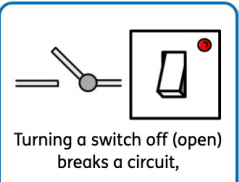
More components, or lower voltage = bulbs dimmer, motors slower and buzzers quieter.




Electrons are the particles that carry the charge through the wires.



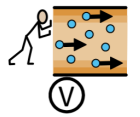
Resistance is when the electrons can't move easily through a circuit. A conductor has little resistance.



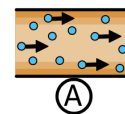
Voltage is a force that pushes the electrons and so makes electricity flow through a wire (it is measured in volts).



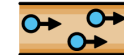Current is the flow of electrical charge around a circuit (this is measured in amps).



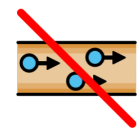Conductor - a material that will allow electrons to flow through easily. Most metals are electrical good conductors.



Insulator - a material that won't let electrons flow through. An example would be rubber.

bulb	motor	buzzer	open switch	closed switch	wire	battery/cell
bulb	motor	buzzer	open switch	closed switch	wire	battery/cell